



***North South University***  
***Department of Electrical & Computer Engineering***


**Lab Report**

<b>Experiment No:</b>	5
<b>Experiment Title:</b>	Design of a 16-bit ALU
<b>Course Code:</b>	CSE332L
<b>Course Name:</b>	Computer Organization & Architecture Lab
<b>Name &amp; ID:</b>	Muhtasin Mashrur Adit , 1821831042
<b>Date of Experiment:</b>	08-12-2020
<b>Date of Submission:</b>	08-12-2020

---


**Equipment:** Logisim tool.

**Block diagram:**

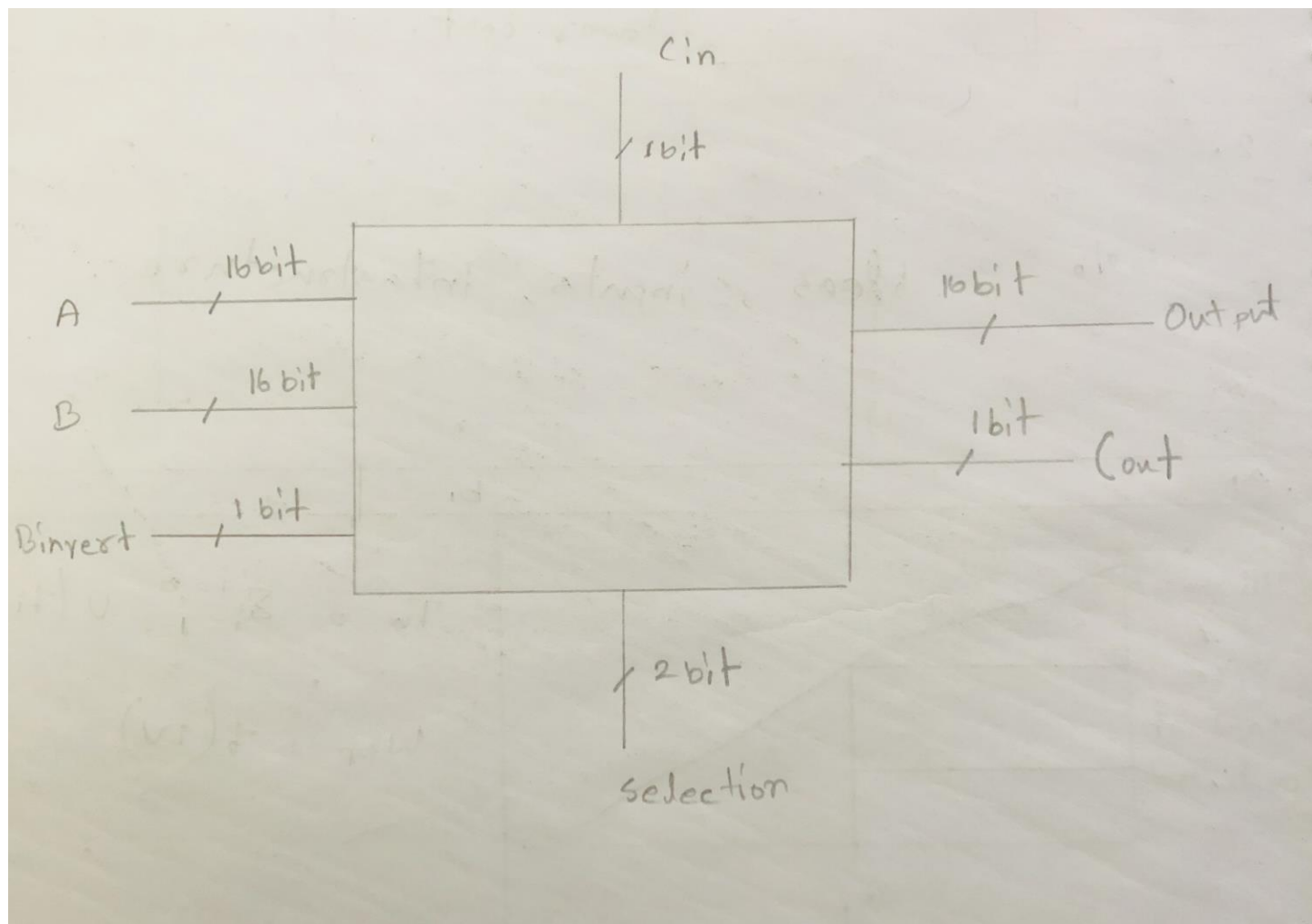

**Figure:** Block diagram of a 16-bit ALU.


### Circuit diagram:

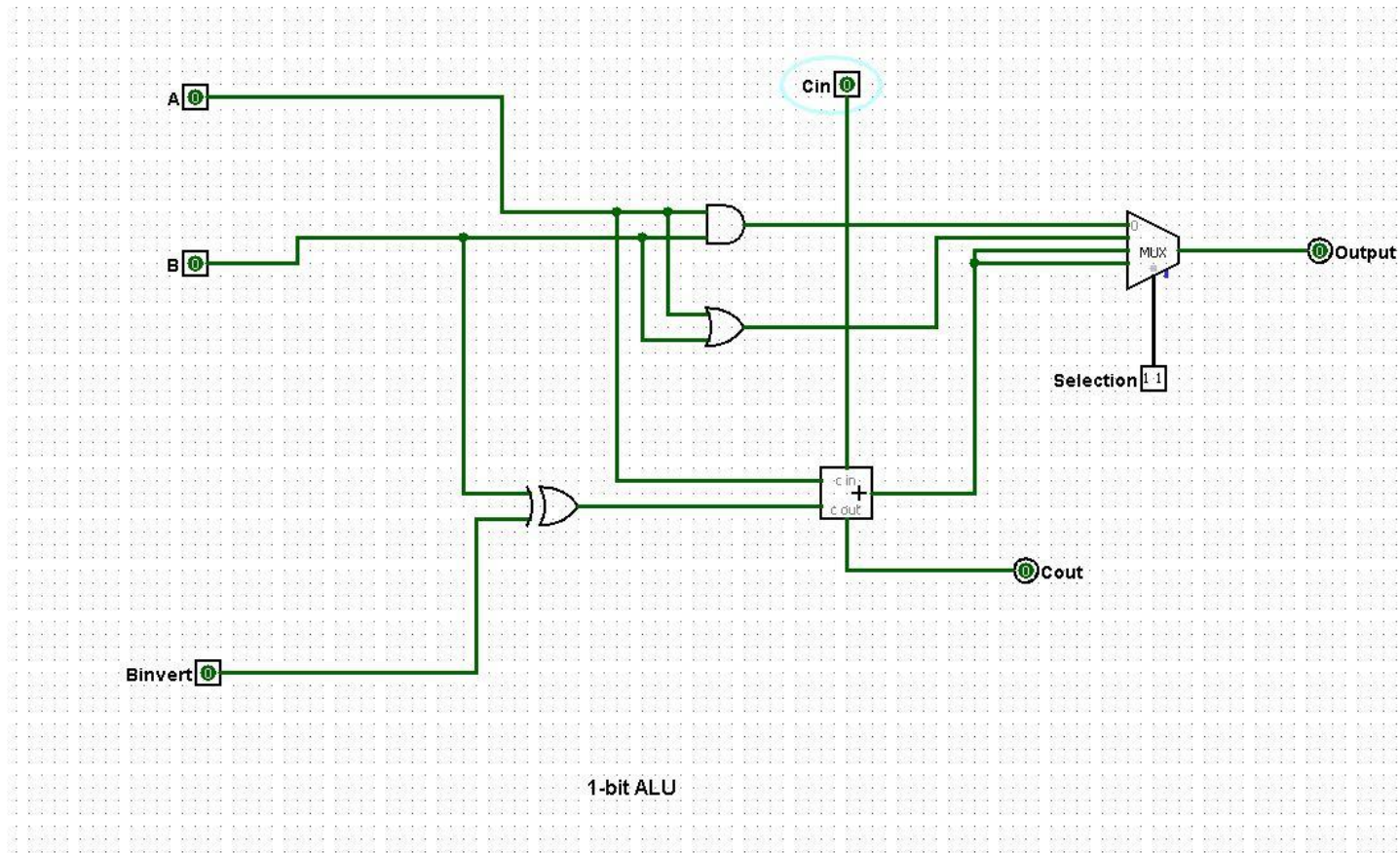

**Figure:** Circuit diagram of a 1-bit ALU.





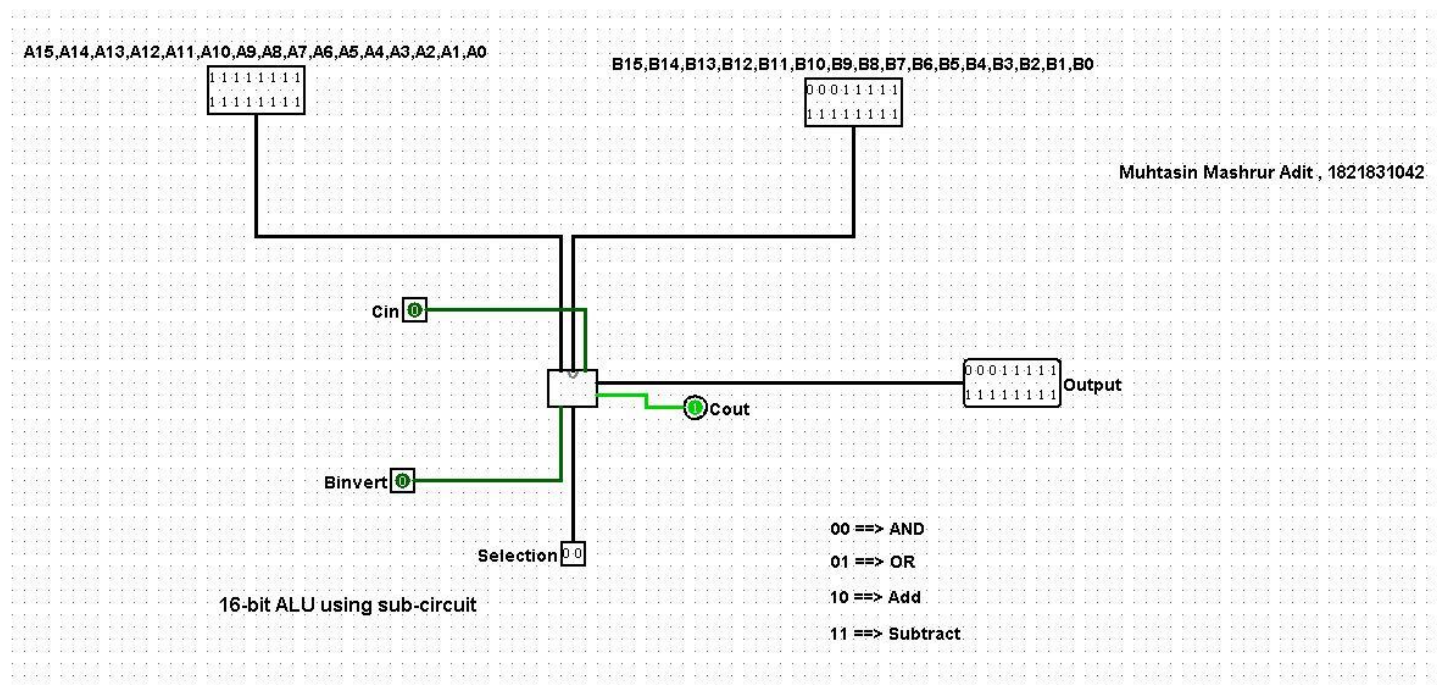

**Figure:** Circuit diagram of a 16-bit ALU using sub-circuit.

**Discussion:** Firstly, in Logisim I've to build a 1-bit ALU. In this circuit I build two arithmetic and two logic functions. Using a 2-bit selection bit multiplexer I separated the circuit for 4 operations. I took an AND gate, an OR gate, an adder circuit and a XOR gate. I took a 1-bit input leveled as Binvert with the B connected in the Xor gate to determine if I want to do addition or subtraction. For addition I will take the input of Binvert 0 and for subtraction I will take 1. Taking 1 as Binvert makes the B's value 1's complement and in the Adder circuit I take the value of Cin 1 to make B 2's complement. Thus, we get more accurate answer in subtraction than the built-in subtractor circuit. For selection bits, 00 is for AND operation, 01 is for OR operation, 10 is for Adder operation and 11 is for Subtraction operation.

Then I take the 1-bit ALU in the 16-bit ALU as sub-circuit. Then I take 16-bit input for A and B. I give the 1-bit connections to the 0-15 labeled sub-circuits respectively from A and B using splitter. The Cout of the previous sub-circuit is connected with the following sub-circuit. From the final sub-circuit, I will get an output labeled as Cout. The outputs of the sub-circuits are respectively connected with the output using a splitter. Then, in the final circuit I took the 16-bit ALU as sub-circuit and take the 16-bit connections for A and B. Manually using the selection bits, Binvert, Cin, we perform 4 different operations in the circuit.